



All JNTU World
Get The Most Out Of Imagineering

S.NO	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
UNIT - I SINGLE STAGE AMPLIFIERS DESIGN AND ANALYSIS			
1	Define an Amplifier?	Remembering	1
2	Describe the single stage amplifier?	Remembering	1
3	Write the advantages of CE configuration over CB and CC configurations?	Applying	1
4	Classify the amplifiers based on different parameters?	Understanding	1
5	Distinguish among three configurations?	Understanding	1
6	Write the advantages of FET over BJT?	Applying	2
7	Arrange the hybrid equivalent model of a CE amplifier?	Remembering	1
8	Discuss a small signal JFET model of a common drain amplifier.	Understanding	2
9	Define various hybrid parameters of a Transistor?	Remembering	1

10	List out the characteristics of Common Emitter amplifier?	Remembering	7
11	Explain the small signal model for common source amplifier?	Understanding	7
12	Write the advantages of Emitter follower?	Applying	7
13	List the benefits of H- Parameters?	Remembering	1
14	Name the typical values of h-parameters for a transistor in CE, CB, CC configurations?	Remembering	1
S.NO	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
15	Explain the typical frequency response of an RC coupled amplifier	Understanding	1
16	Justify why the common emitter amplifier provides 180° phase shift between input and output?	Evaluating	1
17	Construct the approximate h-parameter model for CE amplifier?	Creating	1
19	Define a distortion in amplifiers? Give the classification of distortion?	Remembering	1
20	Define amplitude distortion?	Remembering	1
21	Define frequency distortion?	Remembering	1
22	Define phase or Delay distortion?	Remembering	1
23	Justify the statement, Why the amplitude distortion is called as harmonic distortion?	Evaluating	1
24	Analyze the components affecting the frequency response of RC coupled amplifier at low frequencies?	Analyzing	1
25	Justify the answer, why frequency response of RC coupled amplifier decreases at high frequencies?	Evaluating	1
26	Define the concept of feedback in amplifiers?	Remembering	4
27	Discuss the types of feedback?	Understanding	4
28	Classify the feedback amplifiers based on the type of mixing and type of sampling?	Understanding	4
29	Write the advantages of negative feedback?	Applying	4
30	Distinguish the negative feedback and positive feedback?	Analyzing	4
31	Discuss how does negative feedback reduce distortion in an amplifier?	Understanding	4
32	Define sensitivity of an amplifier?	Remembering	1
33	Analyze the effect of negative feedback on bandwidth?	Analyzing	4
34	Calculate new gain, if An amplifier with stage gain 200 is provided with negative feedback of feedback ratio 0.05.	Analyzing	4
35	Write the relation between lower cut off frequencies with and without feedback.	Applying	4
37	Calculate the feedback ratio, if An amplifier has a gain of 300. When negative feedback is applied, the gain is reduced to 240.	Analyzing	4
38	Estimate the input impedance of the feedback amplifier? If An amplifier with $Z_i = 2K\Omega$ has a voltage gain $A = 200$. If a negative feedback of $\beta = 0.01$ is applied to it.	Evaluating	4
39	Calculate the feedback factor. Express the amount of negative feedback in dB. If the gain of an amplifier is decreased to 10,000 with negative feedback from its gain of 60,000.	Analyzing	4
40	Define an oscillator?	Remembering	4

UNIT-II BJT AND FREQUENCY RESPONSE			
1	Explain the significance of logarithmic scale?	Understanding	3
2	Define “bel” and “Decibel”?	Remembering	3
3	Discuss the half bandwidth calculation of a transistor?	Understanding	3
4	Define dBs?	Remembering	3
5	Define half power frequencies?	Remembering	3
6	Discuss the effect of emitter bypass capacitor on low frequency response of BJT amplifiers.	Understanding	3
7	Sketch the high frequency π model of a transistor and explain in brief.	Applying	3
8	Define f_{α} and f_{β} cut-off frequencies in Hybrid- π model.	Remembering	3

S.NO	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
9	Define square wave testing? What is need for it?	Remembering	3
10	Define f_T ?	Remembering	3
11	Discuss the effect of coupling capacitors on low frequency response of BJT amplifiers.	Understanding	3
12	Write short notes on miller’s theorem.	Creating	3
13	Evaluate the relationship between low frequency h-parameters and high frequency parameters.	Evaluating	3
14	Describe how internal capacitances affect the gain of BJT amplifier.	Evaluating	3
15	Define Band width of an amplifier?	Remembering	3
16	Define gain-bandwidth product?	Remembering	3
17	Define unity-gain frequency?	Remembering	
18	Define voltage gain of the amplifier at f_T ?	Remembering	3
19	Discuss the internal BJT capacitances and explain their effects.	Understanding	3
20	Express power gain in dB	Understanding	3
21	Express voltage gain in dB.	Understanding	3
22	Evaluate the mid-range voltage gain of a transistor?	Evaluating	3
23	Sketch a small signal JFET model of a common drain amplifier.	Applying	3
24	Sketch a voltage divider bias FET network.	Applying	3
25	Write the relationship between the h_{ie} and r_{bb} ’.	Creating	3

UNIT-III MULTIVIBRATORS, CLIPPERS AND CLAMPERS			
1	Define a multivibrator? How many states does it have.	Remembering	2
2	Describe a bistable multivibrator?	Understanding	2
3	Classify the multivibrators?.	Understanding	2
4	Indicate the other names of a bistable multivibrator?	Understanding	2
5	Describe the bistable multivibrator.	Understanding	2
6	Define an ac coupling in multivibrators?	Remembering	2
7	Name the applications of a bistable multivibrator?	Remembering	2
8	Define stable state of a binary?	Remembering	2
9	Define quasi-stable state?	Remembering	2

10	Define loading of a binary? What are its effects on the performance of a binary?	Remembering	2
11	Discuss the purpose of collector catching diodes in multivibrators?	Understanding	2
12	Write the advantage of a self biased binary over fixed biased binary?	Applying	2
13	Define commutating capacitors? Why are they required?	Remembering	2
14	Indicate the other names of commutating capacitors?	Understanding	2
15	Define triggering?	Remembering	2
16	Name the methods of triggering in multivibrators? Distinguish between them.	Remembering	2
17	Define unsymmetrical triggering? Where is it used?	Remembering	2
18	Define symmetrical triggering? Where is it used?	Remembering	2
19	Write the advantages and disadvantages of a direct coupled binary?	Applying	2
20	Discuss about a Schmitt trigger?	Understanding	2
21	List the applications of a Schmitt trigger?	Remembering	2
22	Explain how a Schmitt trigger converts a sine wave into a square wave.	Understanding	2
23	Define the terms i) Upper triggering point(UTP) ii) Lower triggering point(LTP)	Remembering	2
24	Describe a monostable multivibrator?	Understanding	2
25	Indicate the other names of a monostable multivibrator?	Understanding	2

S.NO	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
26	Explain why is monostable multivibrator also called a delay circuit?	Understanding	2
27	List the applications of a monostable multivibrator?	Remembering	2
28	Indicate the type of triggering is used in a monostable multivibrator?	Understanding	2
29	Describe an astable multivibrator.	Understanding	2
30	Write the expression for the period of oscillation of an astable multivibrator when it used as square wave generator.	Applying	2
31	Define clipping in Non-linear wave shaping?	Remembering	2
32	Name the different types of clipping circuits?	Remembering	2
33	Indicate the other names of clipping circuits?	Understanding	2
34	Name the three configurations of clipping circuits?	Remembering	2
35	Indicate the devices required for clipping purposes? Name the commonly used ones.	Understanding	2
36	Define single ended clipping?	Remembering	6
37	Describe about the double ended clipping?	Understanding	6
38	List the applications of circuits?	Remembering	6
39	Define a comparator?	Remembering	6
40	Distinguish between comparator and clipping circuits.	Analyzing	6
41	List the applications of voltage comparators?	Remembering	6
42	Define clamping? What for clamping circuits are used?	Remembering	6
43	Indicate the other names of a clamping circuit?	Understanding	6
44	Define positive clamp?	Remembering	6
45	Define Negative clamp?	Remembering	6

46	Justify why the clamping circuit is also called a dc inserter?	Evaluating	6
47	State clamping circuit theorem.	Remembering	6
48	Define biased clamping?	Remembering	6
49	Discuss about practical clamping circuit?	Understanding	6
50	Distinguish between clipping and clamping?	Analyzing	6
UNIT-IV			
LARGE SIGNAL AMPLIFIERS, LINEAR WAVE SHAPING			
1	Define a linear network?	Remembering	6
2	Define linear wave shaping?	Remembering	6
3	Discuss about a low pass circuit?	Understanding	6
4	Define cut-off frequency?	Remembering	6
5	Evaluate the relation between rise time and bandwidth of a low-pass circuit?	Evaluating	6
6	Define high-pass circuit?	Remembering	6
7	Write the condition for a high-pass circuit, which act as a differentiator?	Applying	6
8	Define peaking?	Remembering	6
9	Justify why RC circuits commonly used compared to RL circuits?	Evaluating	6
10	Explain why f_1 is also called the 3-dB cut-off frequency of an RC high pass filter?	Understanding	6
11	Define the step waveform mathematically. Sketch the step waveform neatly.	Remembering	6
12	Write the expression for rise time $t_{r,in}$ in terms of the time constant RC.	Applying	6
13	Write the expression for rise time $t_{r,in}$ in terms of the cut-off frequency f_2 .	Applying	6
14	Write the condition for an RC low-pass filter to function as a good integrator?	Applying	6

S.NO	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
15	Express how does a capacitor behave for sudden changes in voltage?	Understanding	6
16	Define the terms collector dissipation and conversion efficiency of class A power amplifier	Remembering	6
17	Define a large signal amplifier?	Remembering	5
18	Distinguish between voltage amplifier and power amplifier?	Analyzing	5
19	Write the classification of power amplifiers?	Applying	5
20	Calculate the power that can be dissipated by a transistor at an ambient temperate of $T_A=500C$, given $T_j=2300C$ and $\theta_{JA}=1000C/W$.	Analyzing	5
21	Calculate the junction temperature. If the thermal resistance of a transistor is $100C/W$. It is operated at $T_A=250C$ and dissipates $3W$ of power. Calculated the junction temperature.	A	5
22	Compare the various classes of operation of power amplifiers based on operating cycle.	Evaluating	5
23	Discuss the basic reason for crossover distortion in class-B power amplifiers?	Understanding	5
24	State the advantages of push pull class B power amplifier over class B power amplifier	Remembering	5

25	Define harmonic distortion? How the output signal gets distorted due to the harmonic distortion?	Remembering	5
26	Compare push pull and complementary symmetry class-B power amplifiers.	Evaluating	5
27	Define Heat Sink. What is its function?	Remembering	5
28	Define conversion efficiency of power amplifier.	Remembering	5
29	Define thermal runaway?	Remembering	5
30	Define conversion efficiency of power amplifier.	Remembering	5

UNIT-V
SWITCHING CHARACTERISTICS OF DEVICES

1	Justify how does a diode act as a switch?	Evaluating	6
2	Define dynamic and static resistance of a diode?	Remembering	6
3	Define storage time of a diode?	Remembering	6
4	Define transition time of a diode.	Remembering	6
5	Define reverse recovery time of a diode.	Remembering	6
6	Describe when does a transistor act as a) a closed switch b) an open switch	Understanding	6
7	Define a) Rise time b) storage time c) fall time	Remembering	6
8	Define turn ON time of a transistor?	Remembering	6
9	Translate the term BV_{CBO} ?	Understanding	6
10	Define BV_{CEO} ?	Remembering	6
11	Define the common emitter saturation resistance $R_{CE(sat)}$.	Remembering	6
12	Discuss the three regions of operation of a transistor?	Understanding	6
13	Define the limitations posed by the transistor breakdown voltages?	Remembering	6
14	Explain how does the temperature affect the saturation junction of a transistor?	Understanding	6
15	Define avalanche breakdown.	Remembering	6
16	Define turn-on time of a transistor.	Remembering	6
17	Define delay time of a transistor.	Remembering	6
18	Define zener breakdown.	Remembering	6
19	Define operating point?	Remembering	6
20	Define the turn ON time of a transistor.	Remembering	6

GROUP - II (LONG ANSWER QUESTIONS)

S.NO	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
UNIT-I SINGLE STAGE AMPLIFIERS DESIGN AND ANALYSIS			
1	Evaluate the equations for voltage gain , current gain, input impedance and output impedance for a BJT using low frequency h-parameter model for CE configuration.	Evaluating	1
2	Evaluate the equations for voltage gain, current gain, input impedance and output impedance for a BJT using low frequency h-parameter model for CB configuration.	Evaluating	1

3	Evaluate the equations for voltage gain , current gain, input impedance and output impedance for a BJT using low frequency h-parameter model for CC configuration.	Evaluating	1
4	Evaluate the expression for Ri, Ai, Av and Ro for CE amplifier with un bypassed Re.	Evaluating	1
5	Classify the amplifier circuits based on frequency range, type of coupling, power delivered and signal handled.	Understanding	1
6	State millers theorems. Explain its significance in transistor circuit analysis	Remembering	1
7	Analyze general transistor amplifier circuit using h-parameter model. Derive the expression for Ai,Av,Ri, Ro, Ais, Avs	Analyzing	1
8	Define h-parameters? Why they called so? Define them and what are the benefits of h-parameters	Remembering	1
9	Explain voltage shunt feedback amplifiers & current series feedback amplifiers?	Understanding	1
10	Sketch the block diagram of a feedback amplifier and derive the expressions for gain (1) with positive feedback and (2) with negative feedback. State the advantages of negative feedback.	Applying	1
11	Estimate the values of open loop Gain A and feedback ratio. For the given data iii) An amplifier, with feedback, has voltage gain of 100. When the gain without feedback changes by 20% and the gain with feedback should not vary more than 2%.	Understanding	1
12	(i) Discuss the circuits of voltage shunt and current series feedback amplifier and derive the expressions for input impedance Rif.	Understanding	1
13	Explain the relevant information, how the negative feedback improves stability reduce noise and Increase input impedance?	Understanding	1
14	Design the circuit diagram of CS amplifier. With the help of small signal model, derive the expressions for input impedance, output impedance and voltage gain.	Creating	1
15	(a) Write short notes on miller's theorem. (b) Analyze a single stage transistor amplifier using h –parameters	Applying	1
16	Sketch the circuit diagram of CE amplifier with emitter resistance. Draw its approximate h-parameter model and derive the expression for AI, RI and AV.	Applying	1
17	Show that for voltage shunt feedback amplifier trans resistance gain, Ri and Ro are decreased by a factor $(1+A\beta_v)$ with feedback.	Applying	1

S. No	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
18	Define the following terms in connection with feedback i. Return difference, fb ii. Closed loop gain iii. Open loop gain	Remembering	1
19	Sketch the circuit diagram of CE amplifier with emitter resistance. Draw its approximate h-parameter model and derive the expression for AI, RI and AV.	Applying	1
20	Explain how h –parameters can be obtained from the static characteristics of a transistor.	Understanding	1

UNIT-II
BJT AND FREQUENCY RESPONSE

1	Evaluate the expressions for $f\beta$ and f_T .	Evaluating	3
2	Discuss the effect of coupling capacitor (C_c) on low frequency response of CE amplifier.	Understanding	3
3	Sketch the low frequency small signal model of a transistor in CB and CE configurations and explain significance of each model.	Applying	3
4	Sketch the small-signal high-frequency circuit of a CS amplifier and derive the expression for the voltage gain.	Applying	3
5	Show that (i) $h_{fe} = g_m r_b r_e$ for a Hybrid π model of CE amplifier.	Applying	3
6	Explain how does β and C_c vary with $ I_c $ and $ V_{CE} $.	Understanding	3
7	Explain how does g_m vary with $ I_c $ and $ V_{CE} $, T.	Understanding	3
8	Evaluate the expression for current gain with resistive load.	Evaluating	3
9	Justify why the gain of the amplifier decreases in the low frequency and high frequency range?	Evaluating	3
10	Evaluate the expression for the CE short-circuits current gain A_i as a function of frequency.	Evaluating	3

UNIT-III
MULTIVIBRATORS, CLIPPERS AND CLAMPERS


1	Explain the working of a fixed-biased binary with neat diagram.	Understanding	6
2	Explain the working of a non-saturated binary. What are its drawbacks?	Understanding	6
3	Discuss the different methods of triggering a binary with neat sketches.	Understanding	6
4	Explain the working of a Schmitt trigger with neat sketches.	Understanding	6
5	Evaluate the expressions for UTP and LTP of a Schmitt trigger.	Evaluating	6
6	Explain how hysteresis can be eliminated in a Schmitt trigger.	Understanding	6
7	Explain the working of a collector-coupled monostable multivibrator, With the help of a neat circuit diagram and waveforms,.	Understanding	6
8	Evaluate an expression for the gate width of a monostable multivibrator.	Evaluating	6
9	Explain the working of an astable multivibrator. With help of a neat circuit diagram and waveforms.	Understanding	6
10	Evaluate an expression for the frequency of oscillation of astable multivibrator.	Evaluating	6
11	Show that an astable multivibrator can be used as a voltage to frequency convertor.	Applying	6
12	Construct the circuit of the astable multivibrator and explain how it works.	Creating	6


S. No	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
13	Explain the working of a transistor clipper. With the help of a neat circuit diagram and waveforms.	Understanding	6
14	Explain the working of a two level diode clipping. With the help of a neat circuit diagram.	Understanding	6
15	Explain how a sine wave may be converted into square wave using a clipping circuit.	Understanding	6
16	Explain the working of a simple diode comparator. Draw the output wave form for a ramp input.	Understanding	6
17	Explain the working of a positive clamping circuit. With necessary waveforms.	Understanding	6


18	Explain the working of a Negative clamping circuit. With necessary waveforms.	Understanding	6
19	State and prove the clamping circuit theorem?	Remembering	6
20	Explain the principle of clamping. What is the need for a shunting resistor R in parallel with the diode in the basic clamping circuit?	Understanding	6
UNIT-IV LARGE SIGNAL AMPLIFIERS, LINEAR WAVE SHAPING			
1	Evaluate the expression for maximum conversion efficiency for a simple series fed Class A power amplifier. What are the drawbacks of transformer coupled power amplifiers?	Evaluating	5
2	Explain the method of determination of total harmonic distortion in push pull power amplifiers using five point method.	Understanding	5
3	Define thermal resistance? Explain the thermal electrical analogy related to a transistor with heat sink.	Remembering	5
4	Explain and analyze a transformer coupled class A power amplifier and also define the total harmonic distortion with three point method.	Understanding	5
5	Design the circuit of a series fed class A power amplifier and analyzes it for its efficiency and power dissipation and proves that maximum efficiency is 25%.	Creating	5
6	Sketch the schematic of class B push-pull amplifier with complementary symmetry configuration and explain the working of it.	Applying	5
7	Show that maximum efficiency of Class B amplifier is 78.5%.	Applying	5
8	Show that maximum efficiency of Transformer coupled Class A amplifier is 50%.	Applying	5
9	With a neat diagram explain the principle of operation of class B pushpull amplifier.	Understanding	5
10	Sketch the schematic of class B push-pull amplifier with complementary symmetry configuration and explain the working of it.	Applying	5
11	Explain the operation of low pass RC circuit, and also derive an expression for the output to an exponential input?	Understanding	5
12	Evaluate an expression for the percentage Tilt of the output of a highpass circuit with large time constant excited by a symmetrical square wave with Zero average value.	Evaluating	6
13	Evaluate an expression for the rise time of the output of a low pass circuit excited by a step input.	Evaluating	6
14	Discuss about a low pass RC circuit? Derive an expression of output voltage for square wave input and draw input-output characteristics of this circuit.	Understanding	6
S.No	QUESTION	BLOOMS TAXONOMY LEVEL	COURSEOUTCOMES
15	Sketch the high- pass R-C circuit. Derive for step- voltage response of this circuit and show the input- output characteristics of this circuit.	Applying	6
16	Sketch the response of an RC high-pass for square wave input	Applying	6
17	Explain the response of an RC high-pass filter to behave as a good differentiator.	Understanding	6
18	Evaluate the expression for power output and conversion efficiency of a class A series fed amplifier.	Evaluating	6


UNIT-V			
SWITCHING CHARACTERISTICS OF DEVICES			
1	Explain the phenomenon of “latching” in a transistor switch.	Understanding	6
2	Explain the behavior of a BJT as a switch in electronic circuits. Give an example.	Understanding	6
3	Write a short note on the switching times of transistor.	Applying	6
4	Explain the behavior of a BJT as a switch. Give Applications.	Understanding	6
5	Explain the terms pertaining to transistor switching characteristics. i. Rise time. ii. Delay time.iii. Turn-on time. iv. Storage time v. Fall time. vi. Turn-off time.	Understanding	6
6	Write Short notes on: (a) Diode switching times (b) Switching characteristics of transistors (c) FET as a switch.	Applying	6
7	Explain piecewise linear diode characteristics.	Understanding	6
8	Explain how transistor can be used as a switch in the circuit, under what condition a transistor is said to be „OFF“ and „ON“ respectively.	Understanding	7
9	Discuss how does the temperature affect the saturation junction voltages of a transistor?	Understanding	6
10	Explain how does avalanche multiplication take place in a semiconductor diode?	Understanding	7

GROUP - III (PROBLEMS)

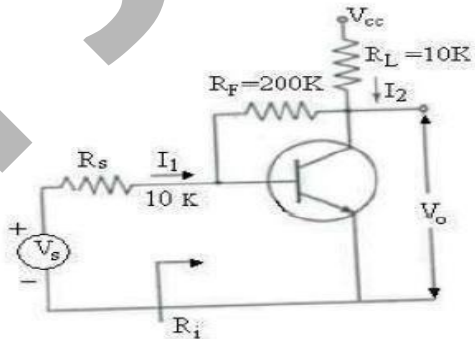S.No	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
UNIT-I			
SINGLE STAGE AMPLIFIERS DESIGN AND ANALYSIS			
1	Compute current gain, voltage gain, input and output impedance of the CB amplifier if it is driven by a voltage source of internal resistance $R_s=1k$. The load impedance is $R_L=1K$. The transistor parameters are $h_{ib}=22$, $h_{fb}=-0.98$, $h_{rb}=2.9 \times 10^{-4}$, $h_{ob}=0.5 \mu A/V$.	Applying	1
2	Calculate A_I , A_V , R_I , R_O of a transistor with $h_{ie}=1.1K$, $h_{fe}=50$, $h_{re}=205 \times 10^{-4}$, $h_{oe}=25 \mu A/V$ is connected in CE configuration as shown in fig. 	Analyzing	1
3	An Amplifier has a voltage gain of 400, $f_1=50Hz$, $f_2=200KHz$ and a distortion of 10% without feedback. Estimate the voltage gain, f_{1f} , f_{2f} and D_f when a negative feedback is applied with feedback ratio of 0.001.	Understanding	


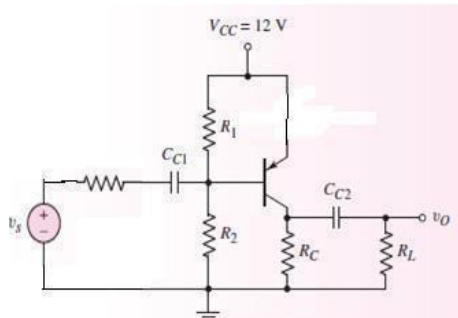
4	Calculate the gain, input impedance, output impedance of voltage series feedback amplifier having $A=300$, $R_i=1.5K$, $R_o=50K$ And $\beta=1/2$.	Analyzing	1
5	 <p>Calculate A_i, R_i, A_v, R_o, A_{vs}, A_{is}, A_p. For circuit shown in below the transistor parameters are $h_{ic} = 1.2K\Omega$ $h_{oc}=25 \mu A/V$ $h_{rc}=1$, $h_{fc}= -101$.</p>	Analyzing	1

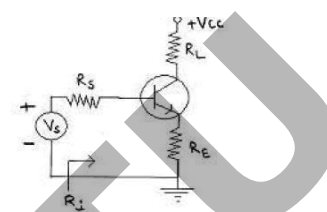S.No	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
6	<p>Evaluate the expression for R_i For the given circuit, shown in the Figure }</p>  <p>b) If $R_1=R_E= 1K\Omega$ and using typical values of h - parameters $h_{ie}=1.1K\Omega$, $h_{fe}=50$, $h_{re}=2.5 \times 10^{-4}$, $h_{oe}=25\mu A/V$. What is the values of R_i.</p>	Evaluating	1
7	Calculate the voltage gain for the common source FET amplifier if , $r_d=100k$ ohm, $g_m=300\mu$, $R_L=10k$ ohm.	Analyzing	1
8	We have an amplifier of 60dB gain. It has an output impedance $Z_O = 10K\Omega$. It is required to modify its output impedance to 500Ω by applying negative feedback factor. Calculate the value of the feedback factor. Also find the percentage change in the overall gain, for 10% change in the gain of the amplifier without feedback.	Analyzing	1
9	<p>An amplifier with open loop voltage gain $A_V = 1000 \pm 100$ is available. It is necessary to have an amplifier whose voltage gain varies by no more than ± 0.1 percent.</p> <p>i. Estimate the reverse transmission factor β of the feedback network used. ii. Estimate the gain with feedback.</p>	Analyzing	1

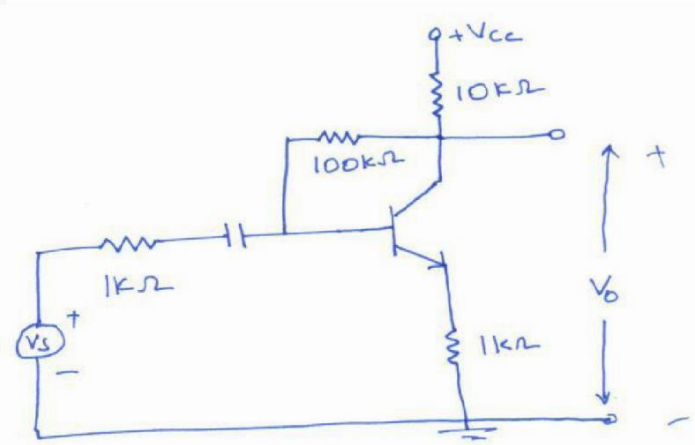10	<p>For the transistor feedback amplifier stage shown $h_{fe}=100$, $h_{ie}=1K$, while h_{re} and h_{oe} are negligible, Estimate the following: $A_v = V_o/V_i$, $A_{vs} = V_o/V_s$, R_{if}, R_{of}.</p> 	Analyzing	1
----	---	-----------	---

S.No	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
UNIT -II (BJT AND FREQUENCY RESPONSE)			
1	Estimate the gain of an amplifier at frequency = 100kHz ,if an Amplifier 3 dB gain is 200 and higher cut-off frequency is 20kHz.	Understanding	3
2	For an amplifier, midband gain is 100 and lower cut-off frequency is 1kHz. Estimate the gain of an amplifier at frequency = 20Hz.	Understanding	3
3	Calculate g_m , $r_{b'e}$, $c_{b'e}$ and $W\beta$, At $I_c = 1mA$ and $V_{ce} = 10V$, a certain transistor data shows $C_c = C_{b'c} = 3pf$, $h_{fe} = 200$ and $W_T = -500 Mrad/sec$.	Analyzing	3
4	Estimate the overall upper 3dB frequency f_H . If four identical amplifiers are cascaded each having $f_H = 100kHz$.Assuming non interacting stages.	Understanding	3
5	A transistor has $h_{ie} = 6k\Omega$ and $h_{fe} = 224$ at $I_c = 1mA$ with $f_T = 80 MHz$ and $c_{b'c} = 12 pf$. Estimate g_m , $r_{b'e}$, $r_{bb'}$ and $c_{b'e}$ at room temperature.	Understanding	
A UNIT-III (MULTIVIBRATORS, CLIPPERS AND CLAMPERS)			
1	The fixed-bias bistable multivibrator uses npn transistors with $h_{fe}=20$.The circuit parameters are $V_{cc} = 12V$, $V_{B} = 3V$, $R_C=1K\Omega$, $R_1= 5 K\Omega$, $R_2 =10 K\Omega$, $V_{CE}(sat) = 0.4V$, and $V_{BE}(sat) = 0.8V$. (a)Estimate the stable state voltages and currents. (b) What is the maximum load the multivibrator can drive, still maintaining one transistor in saturation and the other in cut-off?what is the maximum reverse saturation current I_{CBO} tolerated so that neither of the transistor is at cut-off? If the initial value of I_{CBO} is 10mA at room temperature, what is the maximum temperature at which one device remains off?	Evaluating	6
2	Design fixed bias bistable multivibrator to provide an output with a swing of 10V? b) Design collector coupled fixed-bias Bistable Multivibrator to operate from $\pm 6V$ supply. Given $I_C (sat) = 1mA$, $h_{FE} = 35$. Assume Si transistor?	Creating	6
3	Design a Schmitt trigger circuit to have $V_{CC} = 12v$, $UTP = 6V$, $LTP = 3V$, using two silicon npn transistors with $h_{fe}(\min) = 60$.	Creating	6


4	Estimate the period of output and the frequency of oscillation of an astable multivibrator with $R_1 = R_2 = 25 \text{ K}\Omega$ and $C_1 = C_2 = 0.2 \mu\text{F}$.	Evaluating	6
5	Calculate the input pulse width of mono-stable multivibrator for the design values of $R_C=2\text{k} \Omega$, $R_B=10\text{k} \Omega$; $C=0.1 \mu\text{F}$, $V_{CC}=10 \text{ V}$, $V_{BE}(\text{sat})=0.8\text{V}$.	Analyzing	6
6	In an astable multivibrator circuit shown in the figure 7.4 $R_1=R_2=5\text{k}\Omega$, $R_3=R_4=0.4\text{k}\Omega$ and $C_1=C_2=0.02\mu\text{F}$. Estimate the time period and frequency of oscillators.	Evaluating	6
7	Design a Schmitt trigger circuit using NPN transistors having $h_{FE}(\text{min})=60$. $V_{BE}(\text{Cutoff})=0\text{V}$, $V_{CE}(\text{Sat})=0.2\text{V}$ and $V_{BE}(\text{sat})=0.7\text{V}$. Given $V_{CC}=8\text{V}$ and o/p swing = 6V, $UTP=3.5\text{V}$, $LTP=1.5\text{V}$, $R_1=10\text{K}$ and $R_2=2\text{K}$. Determine R_{C1} , R_{C2} and R_e .	Creating	6
8	Design an astable multivibrator to generate a 5kHz square wave with a dutycycle of 60% and amplitude 12v. Use NPN silicon transistors having $h_{FE}(\text{min})=70$ $V_{CE}(\text{Sat})=0.3\text{v}$, $V_{BE}(\text{Sat})=0.7\text{v}$, $V_{BE}(\text{Cutoff})=0\text{v}$ and $R_C=2\text{K}$. Draw the waveforms seen at both collectors and bases.	Creating	6

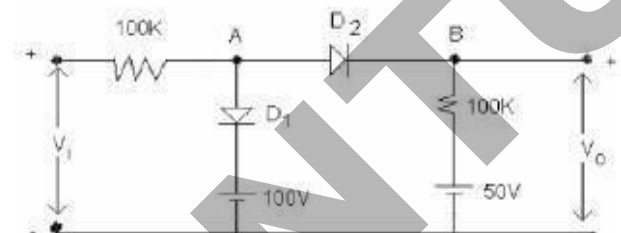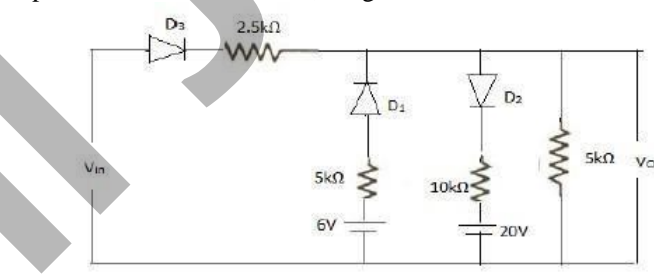S.No	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
9	<p>Sketch the output voltage V_0 to the same scale as the input voltage? If the input voltage V_i to the two-level clipper shown in figure given below varies linearly from 0 to 200V.</p> 	Applying	6
10	<p>Indicate all slopes and voltage levels. Also indicate for each region, the diodes which conduct. For the clipping circuit shown in figure below, make a plot of V_0 versus V_i for the range of V_i from 0 to 50V.</p> 	Understanding	6
11	<p>A 100V peak square wave with an average value of 0V and a period of 20 Sketch the circuit diagram necessary for this purpose. Also, draw the in</p>	Applying put and output wave for	6 ms?

UNIT-IV
(LARGE SIGNAL AMPLIFIERS, LINEAR WAVE SHAPING)

1	Calculate the following for the given data. i. Power dissipation of each transistor ii. Efficiency A complementary push pull amplifier has capacitive coupled load $R_L=8\Omega$, supply voltage of 12V	Analyzing	6
2	Estimate the value of thermal resistance? If the junction temperature of a transistor is 125°C. The total dissipation at a 25°C case temperature is 0.5W and at a 25°C ambient temperature, the total dissipation is 0.2W	Evaluating	5
3	A series fed class A power amplifier operates from a DC source and is applied with a sinusoidal input signal which generates $I_{Bm}=9mA$. Calculate (i) ICQ (ii) VCEQ (iii) PDC (iv) P_{ac} (v) Efficiency.	Analyzing	5

S.No	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
4	Calculate i. Maximum ac power at the load. ii. P_d at maximum ac power iii. Efficiency iv. Maximum P_d at each transistor. For a class B complementary audio frequency power amplifier is as shown in fig.	Analyzing	B
5	Calculate the ac power delivered to the load of $R_L = 2K\Omega$. For a single transistor operates as an ideal class B power amplifier. If dc current drawn from the supply is 25mA.	Analyzing	5
6	Calculate i) Maximum output power ii) Power rating of transistors iii) DC output power. For a complementary symmetry push pull amplifier is operated using $V_{cc} = \pm 10V$ and delivers power to a load $R_L = 5\Omega$.	Analyzing	5
7	A 10HZ symmetrical square wave whose peak-to-peak amplitude is 2V is applied to a High pass RC circuit whose lower 3-db frequency is 5HZ. Calculate and sketch the output waveform?	Analyzing	5

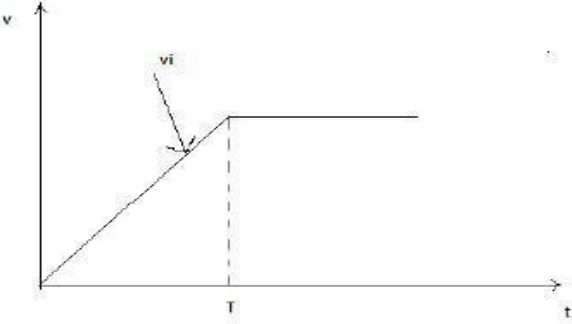8	<p>Sketch the output wave forms for the cases (a) $T = 0.2RC$, (b) $T = 0.2RC$ (c) $T = 5RC$. For the limited ramp shown in figure below is applied to an RC differentiator.</p> 	Applying	5
S.No	QUESTION	BLOOMS TAXONOMY LEVEL	COURSE OUTCOMES
9	<p>A class B push pull amplifier supplies power to a resistive load of 12Ω. The output transformer has a turns ratio of 3 : 1 and efficiency of 78.5%. Calculate : i) Maximum power output ii) Maximum power dissipation in each transistor iii) Maximum base and collector current for each transistor. Assume $h_{fe} = 25$ and $V_{CC} = 20V$.</p>	Analyzing	5
<p>UNIT-V (SWITCHING CHARACTERISTICS OF DEVICES)</p>			
1	<p>A transistor has $f_T = 50 \text{ MHz}$, $h_{FE} = 40$, $C_{b0c} = 3\text{PF}$ and operates with $V_{cc} = 12V$ and $R_c = 500\Omega$. The transistor is operating initially in the neighborhood of the cut-in point. Calculate the base current that must be applied to drive the transistor to saturation in $1\mu \text{ sec}$?</p>	Analyzing	6
2	<p>Design a high speed CE transistor switch operating with two power supplies $V_{cc} = 15V$ and $-V_{bb} = -15V$. The transistor is operating at $I_c = 6mA$, $I_b = 0.5mA$. the static current gain h_{fe} of the transistor is 25. $V_{be(sat)} = 0V$ and $R_2 = 4R_1$. Determine the values of the three resistors R_c, R_1 and R_2</p>	Creating	6
3	<p>Calculate the minimum value of I_b to keep the transistor in saturation when it is in its ON state? Consider a transistor switch in CE configuration operating with $V_{cc} = 18V$ and $-V_{bb} = 0V$ and $V_{ce(sat)} = 0V$. the static current gain h_{fe} of the transistor is 50.</p>	Analyzing	6
4	<p>A silicon transistor is operated at room temperature in the CE configuration. The supply voltage is 6 V, the collector-circuit Resistance is 400Ω and the base current is 20 percent higher than the minimum value required driving the transistor into saturation. Assume the following transistor parameters: $I_{co} = -5\mu A$, $I_{EO} = -2\mu A$, $h_{FE} = 100$, and $r_{bb} = 250$. Calculate $V_{BE}(\text{Sat})$ and $V_{CE}(\text{Sat})$.</p>	Analyzing	6

All JNTU World